

# FT1000 CAT INTERFACE WITH CW

W1AN

The optical switches selected have the low "on" resistance as required by the FT1000 and FT1000D. This interface is for the FT1000 and FT1000D. It may work with other rigs requiring TTL level signals. Use at own risk.

